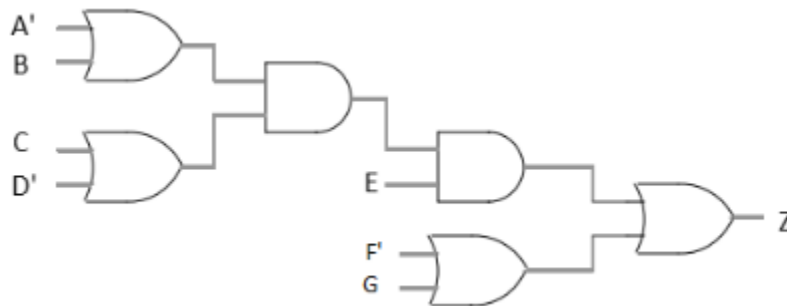




Sheet 6


1. Using AND and OR gates, find a minimum circuit to realize $f(a, b, c, d) = m_4 + m_6 + m_7 + m_8 + m_9 + m_{10}$
 - a. using two-level logic
 - b. using three-level logic (12 gate inputs minimum)
2. Realize $Z = A'D + A'C + AB'C'D'$ using four NOR gates.
3. Realize $Z = ABC + AD + C'D'$ using only two-input NAND gates. Use as few gates as possible.
4.
 - a. Convert the following circuit to all NAND gates, by adding bubbles and inverters where necessary.
 - b. Convert to all NOR gates (an inverter at the output is allowed).



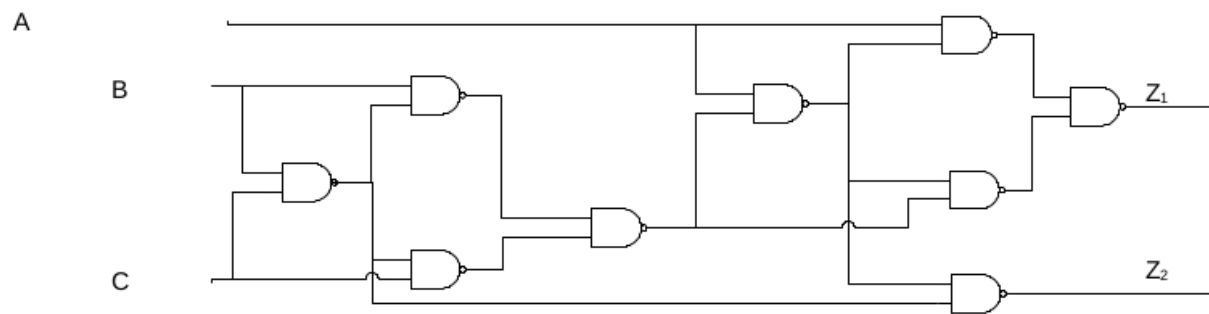5. Find a minimum two-level NAND-NAND circuit to realize the function given in Equations $f = \sum m(6, 7, 8, 9, 13, 14, 15)$
6. $f(a, b, c, d, e) = \sum m(2, 3, 6, 12, 13, 16, 17, 18, 19, 22, 24, 25, 27, 28, 29, 31)$
 - a. Find a minimum two-level NOR-gate circuit to realize f .
 - b. Find a minimum three-level NOR-gate circuit to realize f .
7.
 - a. Find a minimum two-level, multiple-output NAND-NAND circuit to realize $f_1 = \sum m(0, 2, 4, 6, 7, 10, 14)$ and $f_2 = \sum m(0, 1, 4, 5, 7, 10, 14)$.
 - b. Repeat for a minimum two-level, multiple-output NOR-NOR circuit
8. Express the outputs of the following network as functions of the input variables using AND-OR-NOT functions. Check the circuit in the next page

Policies:

- If 2 or more copies are discovered, both parties will receive serious submission penalties.
- No late submission is allowed.



- If 2 or more copies are discovered, both parties will receive serious submission penalties.
- No late submission is allowed.